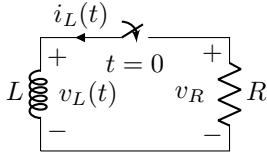


Lecture 26, Mar 18, 2022

Source-Free RL Circuits

- Consider a source-free RL circuit:



- Initial condition: $i_L(0) = I_0$
 - * Since the current of an inductor cannot change abruptly, we find the current
 - * KVL: $v_L - v_R = 0 \implies L \frac{di_L}{dt} + iR = 0$
 - * Solving the differential equation: $\int \frac{1}{i_L} di_L = - \int \frac{1}{\frac{L}{R}} dt \implies \ln(i_L(t)) + K = -\frac{t}{\frac{L}{R}}$
 - * Solution is $i_L(t) = Ae^{-\frac{t}{L/R}}$
 - * Using the initial condition gives $A = I_0$, giving $i_L(t) = I_0 e^{-\frac{t}{L/R}} = I_0 e^{-\frac{t}{\tau}}$ where $\tau = \frac{L}{R}$ is the time constant for an RL circuit
 - Larger time constant means slower decay
 - Similar to τ for a capacitor, the time constant can be found by the intersection of the tangent line at $t = 0$ with the time axis
 - * Voltage: $v_L = L \frac{di_L}{dt} = -RI_0 e^{-\frac{t}{\tau}}$